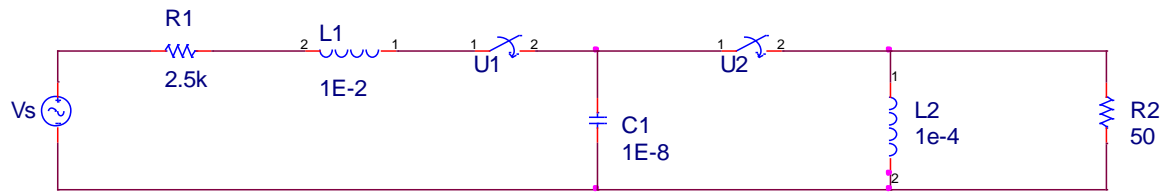


Homework 12

Problem 1) Switched second order circuits




For the above circuit, the source and switches behave as

- 1) The source is turns on at $t = 0$ with a voltage of 20V
- 2) Switch U_1 is closed for $t < 0$ and switch U_2 is open for $t < 0$
- 3) Switch U_1 opens and switch U_2 closes at $t = 15\mu s$


- a. Determine the voltage across the capacitor as a function of time for $t > 0$.
- b. Provide a plot of your result.

(Note: this circuit can be modelled in PSpice using switches, Sw_tOpen and Sw_tClose)

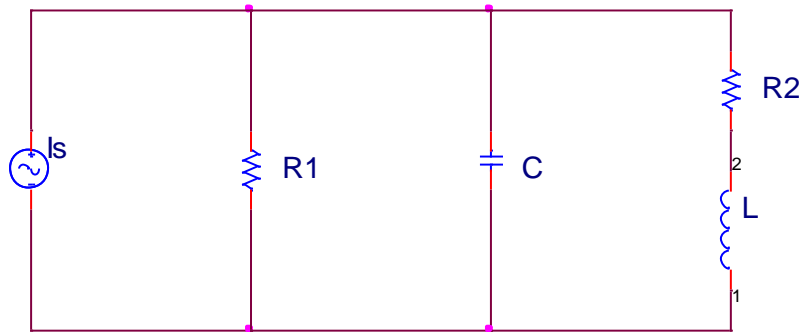Problem 2) More challenging second order circuits



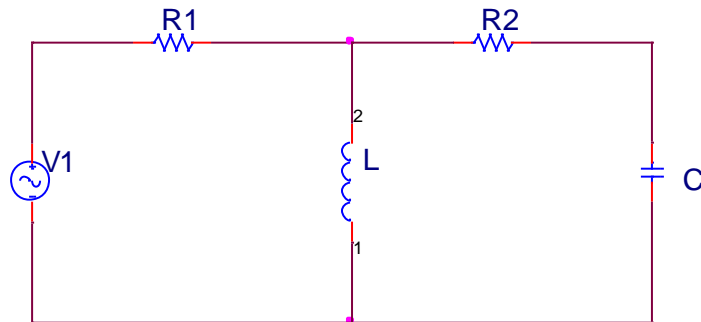- a) For the above circuit, symbolically determine expressions for the differential coefficients α and ω_o .



- b) For the above circuit, symbolically determine expressions for the differential coefficients α and ω_o .

Problem 3) Laplace

a) Find the Laplace transform of

I. $f(t) = 5 - 2.5u(t)$

II. $f(t) = \{5.05e^{(-5E3t)} - 0.05e^{(-1E4t)}\}u(t)$

III. $f(t) = \{2te^{(-5t)} - 10t^2e^{(-5t)} + 10\}u(t)$

IV. $f(t) = \{e^{(-1000t)}[20\cos(10^4t) - 10\sin(10^4t)]\}u(t)$

b) Find the inverse Laplace transform of the following functions. Use partial fraction expansion for V and VI

V. $F(s) = \frac{5}{s^2} + \frac{5}{(s+4)} + \frac{5}{(s^2+4)}$

VI. $F(s) = \frac{s+1}{s^3+2s^2}$

VII. $F(s) = \frac{5}{s^3+7s^2+20s+24}$

1.

- c) Find the poles and zeroes of the above functions. Indicate any repeated poles and complex conjugate poles. (A calculator or Matlab can come in useful)
- d) Plot the poles and zeroes on a real-imaginary plot.